



# EE-254 Final Project

# Team

## Team Members

---

Sai Nayan — 230002058

Akhil — 230002016


Bavith — 230002020

Jagan Mohan — 230002040

Venkat Bhaskar — 230002050
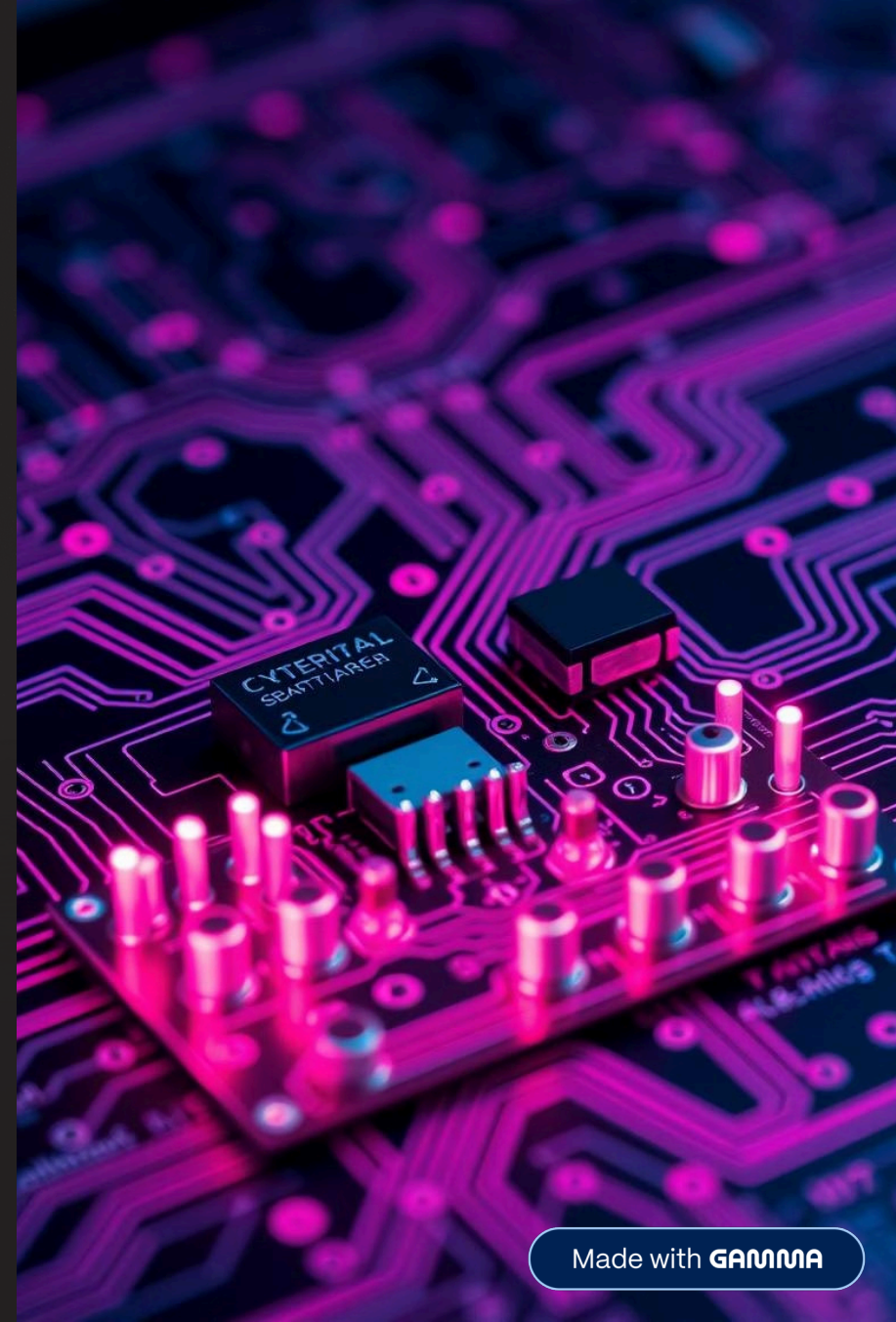
# Problem Statement

Design a Wein bridge oscillator to generate a 1.2 MHz sinusoidal signal using a transistor based amplifier configuration.



# About

## Overview

A Wien-bridge oscillator built with BJTs combines a frequency-selective feedback network (the “Wien bridge”) with a two-stage transistor amplifier and an automatic amplitude stabilization element.

- Consists of a lead-lag RC network: a series RC branch feeding into a parallel RC branch.
- At its resonant frequency
- $f = 1/(2\pi RC)$
- The bridge has unity gain and zero phase shift, so it passes only that frequency back into the amplifier.

## Few Advantages:

### *Single-Supply Operation*

- Runs happily on a single 5–15 V rail; no need for dual  $\pm$  supplies. That makes it ideal for battery-powered or portable test gear.


### *Wide Frequency Range*

- With modern low-tolerance capacitors and small resistor values you can cover from a few kHz up into many MHz with the same topology—just scale  $R/C$ .



# Circuit Diagram

## 2-stage Transistor Amplifier

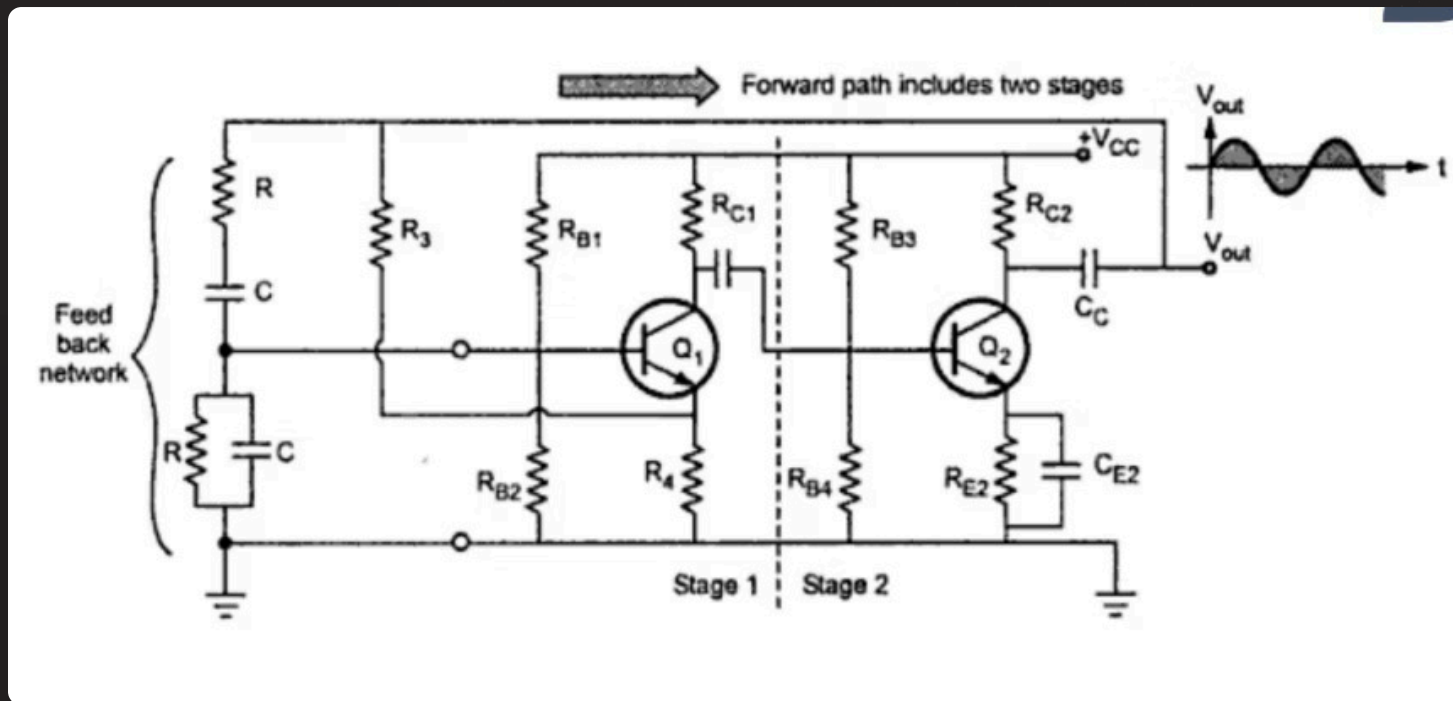

Q1: Amplifier Stage

Q2: For automatic gain control

# Key Assumptions

## Why is $V_{ce}$ set to 50% of $V_{CC}$ ?

- **Maximum Output Swing:** Centering  $V_{CE}$  at half of  $V_{CC}$  allows the output signal to swing equally in both directions (towards saturation and cutoff) without distortion, maximizing the undistorted output amplitude.
- **Stability:** This setting provides the best margin against variations in transistor parameters and temperature, ensuring the transistor remains in its active region during operation.


## Why is $V_{re}$ set to 10% of $V_{CC}$ ?

- **Good Bias Stability:** A larger  $V_{RE}$  (relative to  $V_{BE}$ ) makes the bias point less sensitive to variations in  $V_{BE}$  and transistor beta ( $\beta$ ), improving thermal stability.
- **Predictable Operation:** It provides a straightforward way to select  $R_E$  for a given emitter current.

## Calculations:

Setting  $V_{cc}$  as 12V.

Current gain for this transistor is 110.

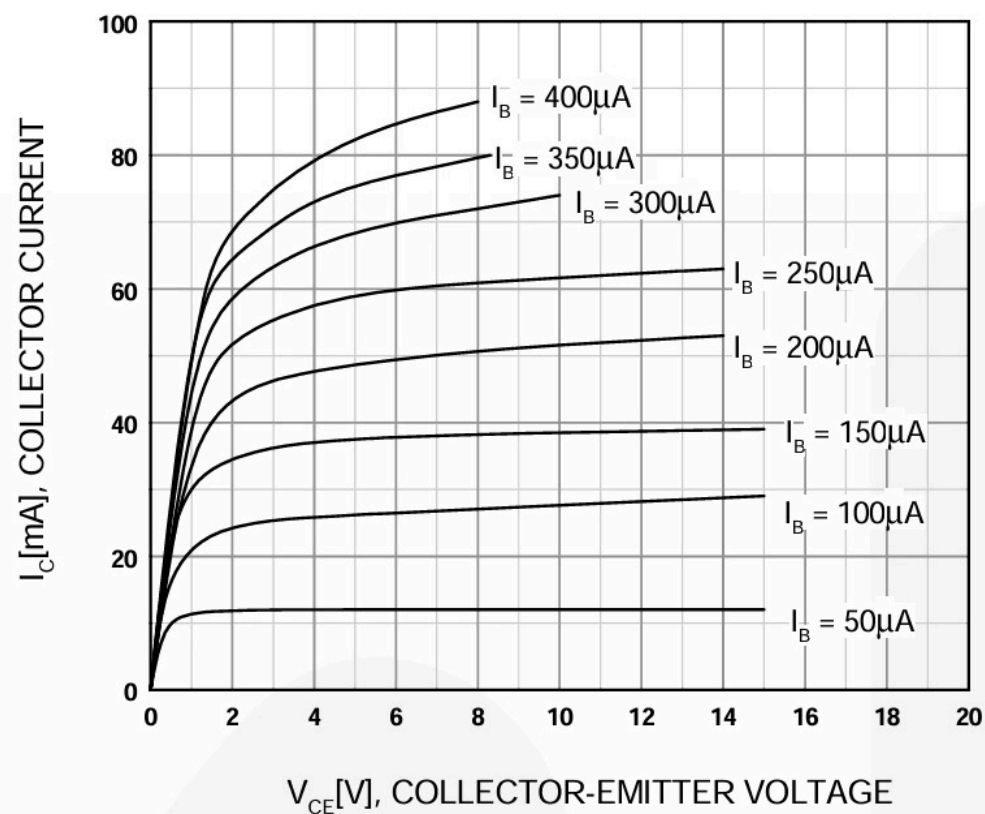

For  $I_b = 13.6\mu A$ , value of  $I_c$  in active region is 1.5mA. This can also be verified by the datasheet.

docs.google.com



- For Q point we are setting  $V_{ce}$  to 50% of  $V_{cc}$  which is equal to 6V.
- Setting  $R_e$  as 10% of  $V_{cc}$  which is equals to 1.2V.
- $V_{re} = I_c \times R_e$ , from here  $R_e = 800$  ohm (standard value taken as 1kohm).
- $V_{rc} = V_{cc} - V_{ce} - V_{re} = (V_{cc} = 12V, V_{ce} = 6V, V_{re} = 1.2V)$ , we get  $V_{rc}$  as 4.8V.
- $R_c = V_{rc}/I_c = 3.2k$  ohm (standard value taken as 3.3k ohm).
- $I_b = I_c/h_{fe}$  which is equal to 13.6 $\mu A$ .
- Current through  $R_2$  is 11  $I_b$ , and current through  $R_6$  is 10  $I_b$ .
- $V_b = V_{re} + V_{be}$ . ( $V_{be} = 0.6V, V_{re} = 1.2V$ ), we get  $V_b$  as 1.8V.
- $R_2 = V_{cc} - V_b / 11I_b = 68k$  ohm.
- $R_6 = V_b / 10I_b = 12k$  ohm.

## Selecting Proper $R_I$ :

For a gain of 110, the required  $R_I$  is 4k ohm.

## Continued...

### Design of coupling capacitance:

- $X_{C1}$  should be less than the input impedance of the transistor. Here,  $R_{in}$  is the series impedance. Then  $X_{C1} \leq R_{in}/10$ . Here  $R_{in} = R_1 // R_2 // h_{fe}$ . (  $R_1 = 68\text{ k}$  ,  $R_2 = 12\text{ k}$  ,  $h_{fe} = 110$  , implies  $R_{in}$  is  $108.8376$ ).
- From this the required capacitance must be greater than **5.1uF** (for a lower cutoff frequency of 200Hz), standard value is **10uF**.
- Similarly,  $X_{C2} \leq R_{out}/10$  , where  $R_{out} = R_C$ . Then  $X_{C2} \leq 330\text{ohm}$ .
- This implies we get C value greater than **2.4uF**(or a lower cutoff frequency of 200Hz), standard value is **4.7uF**.

### Design of bypass capacitance:

- To bypass the lowest frequency (say 200 Hz),  $X_{C_E}$  should be much **less than or equal** to the resistance  $R_E$ .
- $X_{C_E} \leq R_E/10$  which is  $X_{C_E} \leq 800/10$  i.e.  $X_{C_E} \leq 80$ .
- Further, we should get capacitance value as more than **10uF**.



## Design of Wein bridge circuit:

$$R_3 \left[ \frac{R_2}{1 + j\omega C_2 R_2} \right] = R_4 \left[ R_1 - \frac{j}{\omega C_1} \right]$$

It can be written as,

$$R_2 R_3 = R_4 (1 + j\omega C_2 R_2) (R_1 - j/\omega C_1)$$

Or

$$R_2 R_3 - R_4 R_1 - R_2 R_4 + \frac{j R_4}{\omega C_1} - j\omega C_2 R_2 R_1 R_4 = 0$$

By separating real and imaginary terms we can get

$$R_2 R_3 - R_4 R_1 - \frac{C_2}{C_1} R_2 R_4 = 0$$

$$\text{or } \frac{C_2}{C_1} = \frac{R_3}{R_4} - \frac{R_1}{R_2}$$

$$\frac{R_4}{\omega C_1} - \omega C_2 R_2 R_1 R_4 = 0$$

..

$$\omega^2 = \frac{1}{C_1 C_2 R_1 R_2}$$

$$\omega = \frac{1}{\sqrt{C_1 C_2 R_1 R_2}}$$

$$f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

If  $C_1 = C_2 = C$  and  $R_1 = R_2 = R$ , then

$$f = \frac{1}{2\pi CR}$$


$$\text{and } R_3 = 2R_4$$

Using above equations to get the frequency of **1.2 MHz**, the chosen values are:


- **$R_{10}=R_{11}= 10\text{k ohm.}$**
- **$C_5= C_6= 13.2\text{pF.}$**
- **$R_1 = 4.7\text{k ohm.}$**
- **$R_{12} =1\text{k ohm.}$**

# Simulations:

## Output Waveform-

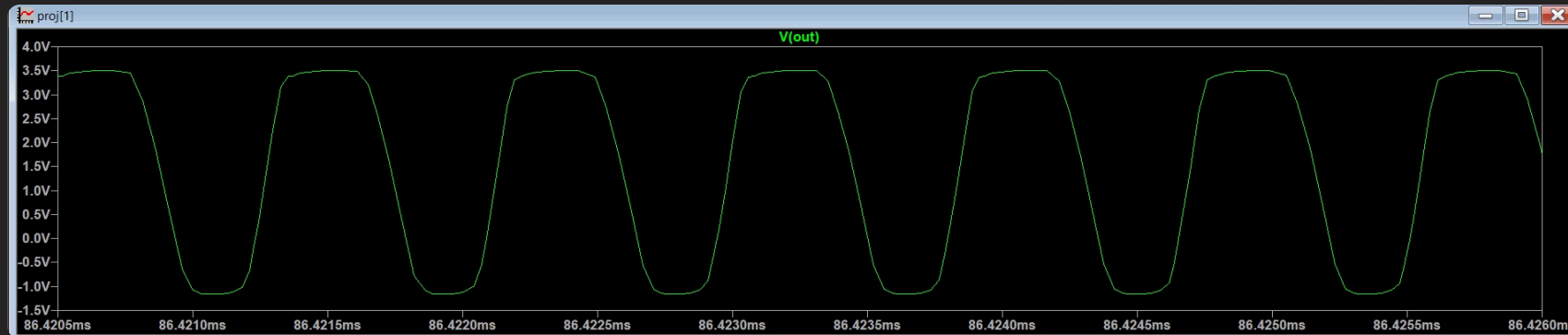

## Schematic:

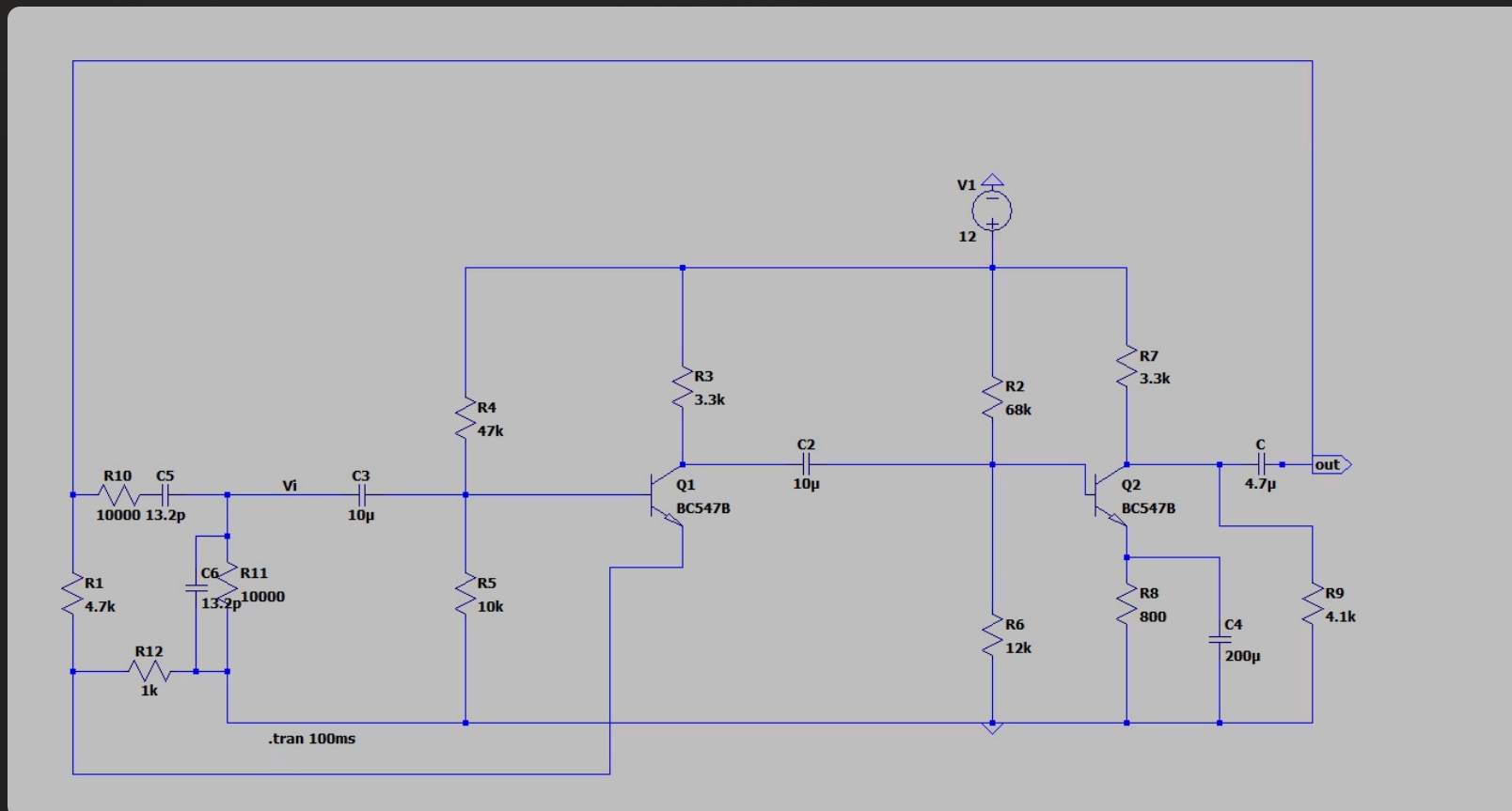

# Observations:

- Although, the circuit is designed for creating a perfect sine wave. Practically, there were a lot of parasitics (non-Ideality) involved such as resistances of wires, Capacitors, non-Ideality of BJT.
- Difference between the LTspice simulation results and the DSO output is observable, for which the possible reasons might be inaccurate resistances(Different from labelled), Non-Ideality of Breadboard, etc. ..